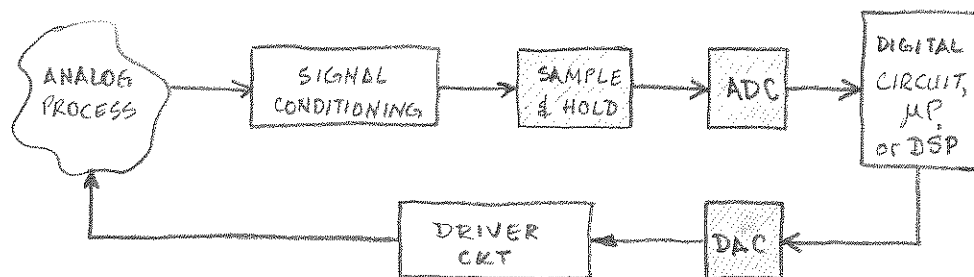


## DATA CONVERSION CIRCUITS

Typical process control configuration




### Sample & Hold Circuits (S/H)

- Provide a stable DC signal for the conversion time of an ADC.
- Should operate at the required sampling rate required by application:
  - Nyquist criterion: The minimum rate at which a signal can be sampled to allow its unique reproduction is twice the maximum frequency component of the input signal.


$$f_s \geq 2 \times f_{i_{\max}}$$

- Violating the Nyquist criterion produces a spectral folding in the reproduced signal called aliasing.

• Idealized S/H circuit:

 

 - Switch  $S$  is closed during sample period.
- When  $S$  is opened after sampling, capacitor  $C$  holds the last value of  $V_i$  during sampling.



SP = Sampling period

$t_s$  = Sample time


$t_h$  = holding

$t_i$  = period of  $V_i(t)$

usually  $t_s \ll SP \ll t_i$

Idealized behavior (assumes  $R_i = 0$  and  $R_L = \infty$ )

 
- A more realistic representation of a S/H circuit



$R_i$  = Output impedance of  $V_i(t)$  & switch resist.

$R_L$  = Input impedance of  $V_o(t)$  & capacitor leak

 - Implementations try to make  $R_i \rightarrow 0$  and  $R_L \rightarrow \infty$
- Basic Open-Loop S/H circuit



- NMOS used as switch

- Voltage follower provide



- Low  $R_o$
- High  $R_i$

- Charging time constant

$$\tau_c = R_a C = (R_o + r_{ds_{on}}) C \rightarrow \text{small}$$

- Discharging time constant  $\tau_d = R_b C = (R_i + r_{leak}) C \rightarrow \text{large}$


- Diode Bridge S/H circuit

  


- When  $|V_i(t)| < V_1 - V_f$ ,  $C$  charges to  $V_i$  through  $R$ .  $V_o(t) = V_i(t)$
- When  $V_i(t) < V_o(t-1)$ ,  $C$  discharges through  $R$ .  $V_o(t) = V_i(t)$

- Usually S/H circuit should be physically close to ADC
- Capacitors of polycarbonate, polyethylene, or polystyrene are recommended for  $C$ . DO NOT USE TANTALUM CAPACITORS
  - This to reduce the effect of dielectric absorption

## S/H Parameters

 

- Acquisition time: Time required for  $C$  to charge to a specific percentage of  $V_i(t)$ 
  - Typical specs call for  $\pm 0.01\%$  i.e.  $t_{\alpha 98} = 9R_a C$
  - For small  $R_a$  values, critical factor is opamp slew rate ( $I_{o\max}$ )
- Aperture delay: Time between hold command and switch aperture
- Droop Rate: Rate of decay of stored voltage
- Settling time: Time for output to settle after a hold command
- Slew Rate: Maximum rate of change of the stored voltage.
- Other: Pedestal error, Feedthrough
- Closed-loop S/H circuit

 

- High accuracy low-frequency tracking
- Feedback loop forces output to track input

- Provides fast acquisition and settling times.
- More strict settling time requirements than open-loop S/H

DAC Input and ADC Output

- Commonly in NATURAL BINARY

$$N = a_{-1} 2^{-1} + a_{-2} 2^{-2} + \dots + a_{-n} 2^{-n} = \sum_{i=1}^n (a_{-i} 2^{-i})$$

$$a_i \in \{0, 1\}$$



← Left justified format

A voltage value is obtained as  $V_o = N V_{FS}$


$V_{FS}$  = Full scale voltage (maximum value)

$$V_{o(FS)} = (1 - 2^{-n}) V_{FS}$$

LSB change  $V_{LSB} = \frac{V_{FS}}{2^n}$  : Defines converter resolution

- An n-bit DAC has  $2^n$  coded levels.


Example: A 3-bit DAC, Transfer function

 

- Note the maximum output value  $V_{o(FS)} < V_{FS}$  by 1 LSB
- This example is an unipolar output DAC: Only positive voltage values



 - Transfer Function of an unipolar ADC with  $-\frac{1}{2}$  LSB offset at zero scale



- Quantization: Process of digitizing ADC samples into discrete ranges
- Quantization Error: Introduced by quantization process.
- Transfer function offset: shifts transfer function to reduce quantization error

$$\text{offset} = -\frac{1}{2} \text{LSB} \rightarrow \text{Q.E.} = \pm \text{LSB}/2$$

$$\text{offset} = 0 \rightarrow \text{Q.E.} = 1 \text{LSB}$$

- Signal-to-noise ratio (SNR) of an ADC: Measures proportion of noise introduced by quantization process

$$\text{SNR} = 10 \log(\text{Signal}/\text{Noise})$$

$$\text{Signal} = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} s^2(t) dt$$

$$\text{Noise} = \int_{-\infty}^{\infty} q^2 p(q) dq$$

$p(q) \leftarrow$  Probability density function of error.

For an ADC with  $-\frac{1}{2}$  LSB offset  $\text{Noise} = \frac{V_{FS}^2}{3 \times 2^{2(n+1)}}$

- Increasing number of bits increases SNR


# • Converter Specifications

- Resolution: Smallest incremental change in
  - Input (detection) in an ADC
  - Output (resolved) in DAC




$$\text{Resolution} = \frac{1}{2^n} \times 100\%$$

- Accuracy: Worst case deviation of output with respect to actual input value. Includes errors from.
  - Quantization
  - System noise
  - Non-linearity
  - Offset error

DAC nonlinearity

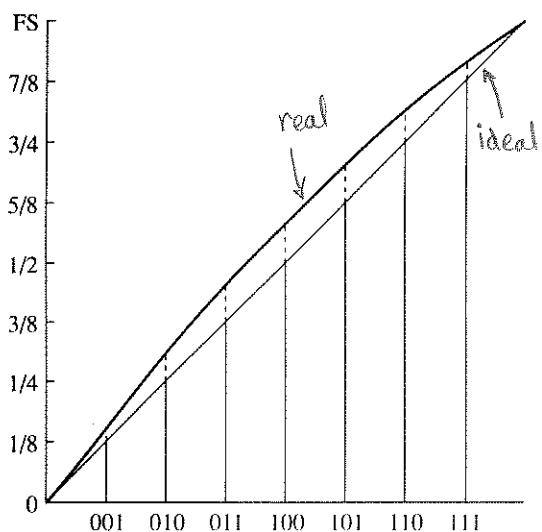


ADC nonlinearity

   
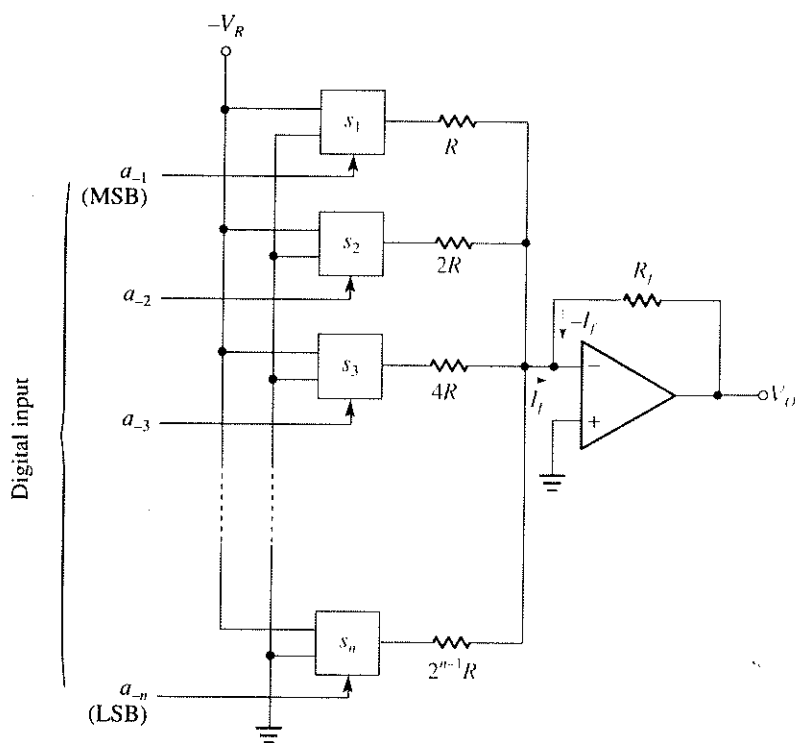
## Digital-to-Analog Conversion

- Simplest circuit: using binary-weighted resistors



$$i = 1, 2, \dots, n$$

$$R_i = 2^{i-1} R$$

$$I_f = \sum_i I_i$$


$$I_f = \frac{-2 V_R N}{R}$$

$$\text{So } V_o = -I_f R_f$$

$$V_o = \frac{2 R_f}{R} V_R N$$

\* Impractical because of values of Resistors.


- Ladder type DAC

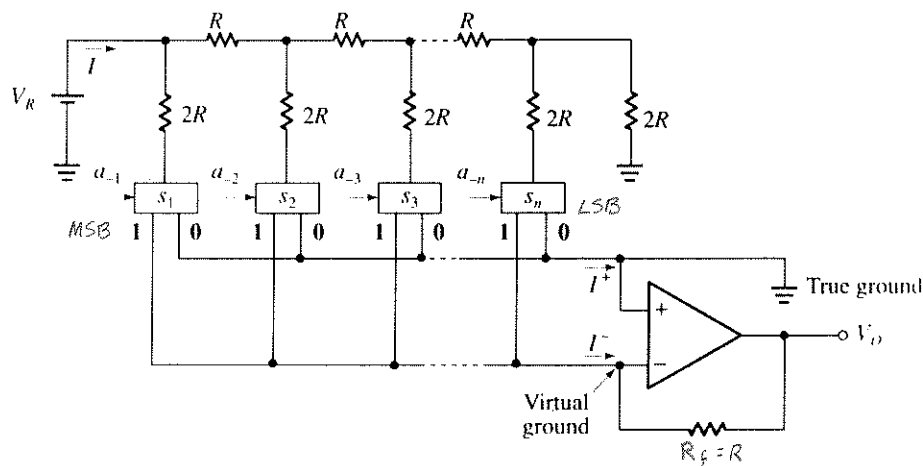

$$I = V_R / R$$

- Binary weighted currents on each branch
- Easy to implement because only two different resistors:  $R$  &  $2R$


Multiplying DAC: Uses a variable  $V_R$

 

Requires external current-to-voltage converter to provide voltage output
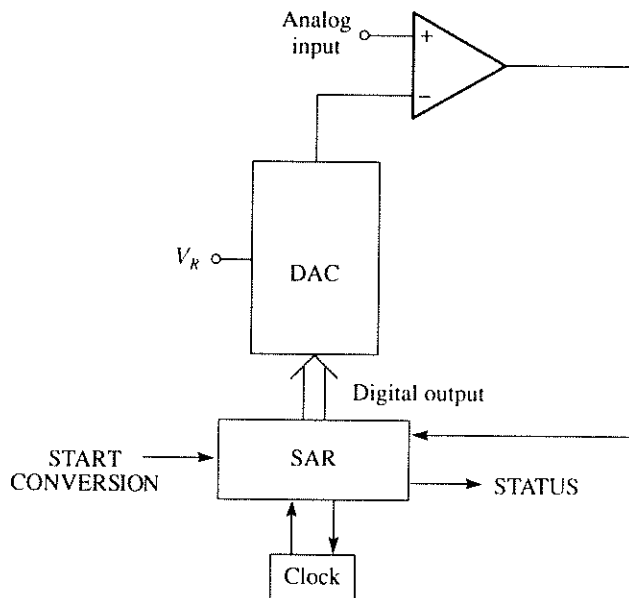
## Analog-to-Digital Converters

- Successive approximation ADC:
  - Bit are sequentially set from MSB to LSB until conversion is complete.




- Only the bits making  $V_c < V_i$  are left on in each step
- Take  $n$  clock cycles to complete a conversion


- Dual-slope ADC:

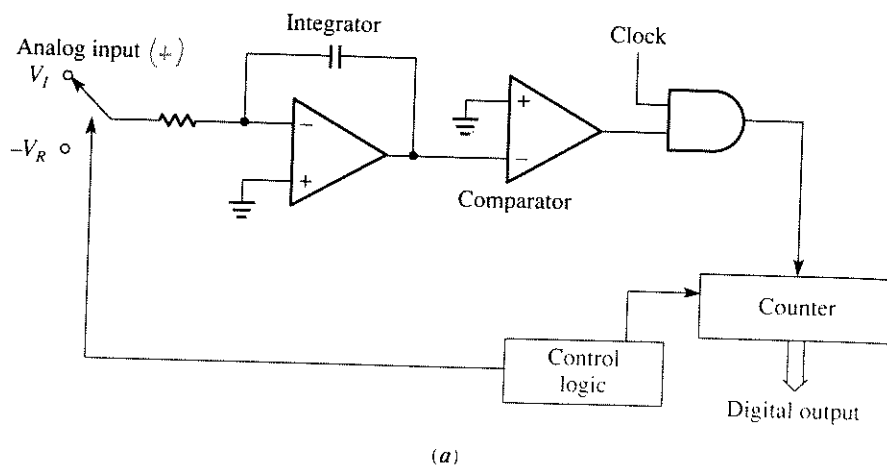- Converts analog input to a time function
- Time function controls counting time of a counter which provides a digital output





(a)

 


(b)


$$n = \frac{N}{V_R} V_I$$

$t_1 \neq f_c$

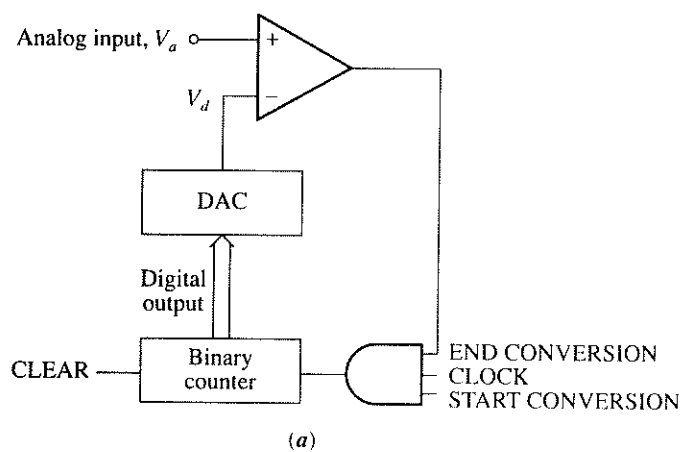\* Counting ADC : Replaces SAR by counter



(a)

 


(b)


Flash ADC: Simplest and fastest. Also the largest in terms of hardware.  
Requires  $2^n$  comparators for an  $n$ -bit conversion

Encode = 0  $\rightarrow$  Sample mode

 
Encode = 1  $\rightarrow$  Freeze mode and output encoded into binary



### Conventional Data Conversion:

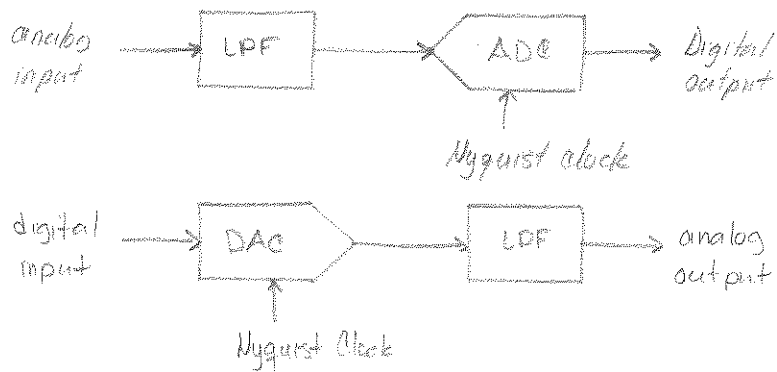

### Oversampling Data Conversion:

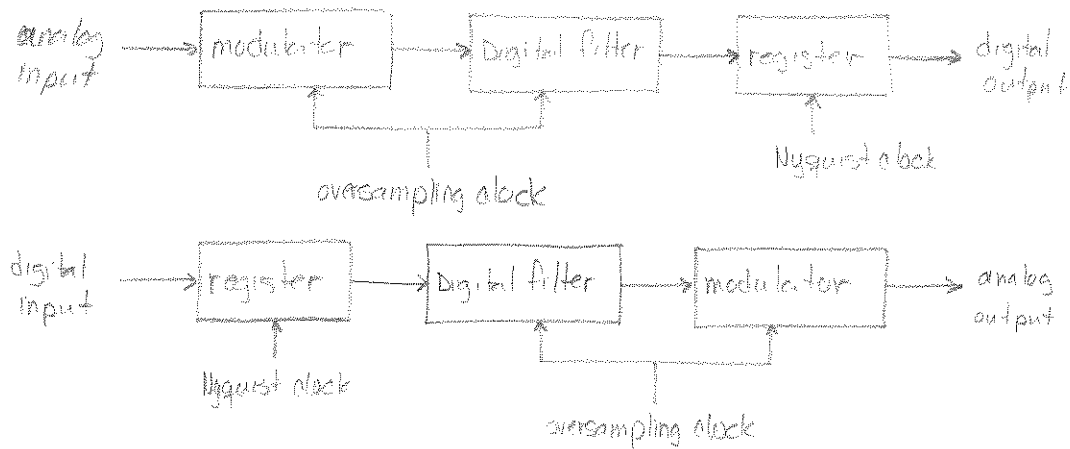

### Virtues of oversampling converters:



- High tolerance analog components
- Trade resolution in time for resolution in amplitude
- Eliminates the need for abrupt cut-off in the analog filters.
- Extensive use of DSP.

An important remark is that there is NO one-to-one correspondence between the input and output signal, and hence no classical methods of characterization can be used. Instead techniques of communications are used to describe the performance of oversampled data converters.

# Sigma-Delta Modulator Structure

$\Sigma\Delta M$ : Sigma-Delta Modulator


I. Basic Principles:

  

STF:  $H_S(z) = \frac{H(z)}{1 + H(z)}$  (LPF)

NTF:  $H_N(z) = \frac{1}{1 + H(z)}$  (HPF)

II. 1st Order  $\Sigma\Delta M$

 

STF:  $H_S(z) = z^{-1}$   
 NTF:  $H_N(z) = 1 - z^{-1}$  }  $H(z) = \frac{z^{-1}}{1 - z^{-1}}$  (integrator)

Time domain:

$$y(n) = x(n-1) + e(n) - e(n-1)$$

$x(n)$	$u(n)$	$v(n)$	$y(n)$
		0	0
2/8	2/8	2/8	+1
2/8	-6/8	-4/8	-1
2/8	10/8	6/8	+1
2/8	-6/8	0	-1
2/8	10/8	10/8	+1
2/8	-6/8	4/8	+1
2/8	-6/8	-2/8	-1
2/8	10/8	8/8	+1

average 2/8

### III. 1<sup>st</sup> Order $\Sigma\Delta$ Implementation

